

Digital Design Lab Report

Xiaokun Du

February 2023

1 Arithmetic logic unit (ALU)

Write, as a SystemVerilog module with the name `alu`, a behavioural description of an arithmetic logic unit.

The data inputs, `SrcA` and `SrcB`, and the data output, `ALUResult`, are 8-bit vectors. The ALU-Control input is a 2-bit vector.

The 1-bit output flag `Zero` = 1 if `ALUResult == 0`, else `Zero` = 0. The ALU carries out bitwise logical operations, and addition and subtraction operations, as specified in the table below.

1.1 Module Code

```
module alu(input logic [7:0] SrcA,
          input logic [7:0] SrcB,
          input logic [1:0] ALUControl,
          output logic [7:0] ALUResult,
          output logic Zero);

always_comb
case (ALUControl)
2'b00 : ALUResult = SrcA & SrcB;
2'b01 : ALUResult = SrcA | SrcB;
2'b10 : ALUResult = SrcA + SrcB;
2'b11 : ALUResult = SrcA - SrcB;
default : ALUResult = 8'bx;
endcase

assign Zero = (ALUResult == 8'b0);
endmodule
```

1.2 Testbench Code

```
`timescale 1ns/1ps
`include "alu.sv"

module alu_tb;
```

```

logic [7:0] t_SrcA, t_SrcB;
logic [1:0] t_ALUControl;
logic [7:0] t_ALUResult;
logic t_Zero;

alu uut (t_SrcA, t_SrcB, t_ALUControl, t_ALUResult, t_Zero);

initial begin
    $dumpfile("alu_tb.vcd");
    $dumpvars(0, alu_tb);
    // Stimulus generator
    t_SrcA = 8'h05; t_SrcB = 8'h0A;
    t_ALUControl = 2'b00; #20;
    t_ALUControl = 2'b01; #20;
    t_ALUControl = 2'b10; #20;
    t_ALUControl = 2'b11; #20;
end

initial begin // Response monitor
    $monitor ("t_ALUControl = %b t_SrcA = %h t_SrcB = %h t_ALUResult = %b t_Zero = %d",
        t_ALUControl, t_SrcA, t_SrcB, t_ALUResult, t_Zero);
end

endmodule

```

1.3 Simulations

The simulation result using Icarus Verilog is as following:


VCD info: dumpfile alu_tb.vcd opened for output.

```

t_ALUControl = 00 t_SrcA = 05 t_SrcB = 0a t_ALUResult = 00000000 t_Zero = 1
t_ALUControl = 01 t_SrcA = 05 t_SrcB = 0a t_ALUResult = 00001111 t_Zero = 0
t_ALUControl = 10 t_SrcA = 05 t_SrcB = 0a t_ALUResult = 00001111 t_Zero = 0
t_ALUControl = 11 t_SrcA = 05 t_SrcB = 0a t_ALUResult = 11111011 t_Zero = 0

```

 The simulation results using GTKWave is as following:



2 Register File

The register file has sixteen 8-bit registers. The register with address 0 always contains the value 0. The other 15 registers can have values written into them through the WD3 port.

The contents of any two of the registers (with addresses specified by the 4-bit inputs RA1 and RA) are continuously output as RD1 and RD2. On the positive edge of the clock, if write_enable is asserted, and A3 \neq 0, the input ALUResult is written into the register at address A3 through the WD3 port. The module includes an output port cpu_out, which continuously outputs the contents of the register at address 15. This will form the main external output of the microprocessor.

2.1 Module Code

```
module reg_file(input logic [3:0] RA1, RA2, WA,
               input logic [7:0] ALUResult,
               input logic clk, write_enable,
               output logic [7:0] RD1, RD2, cpu_out);

    logic [7:0] rf [0:15];
    logic [3:0] zero;

    assign RD1 = rf[RA1];
    assign RD2 = rf[RA2];
    assign cpu_out = rf[15];

    always_ff @(posedge clk)
    if (write_enable && WA > 0)
        rf[WA] = ALUResult;

endmodule
```

2.2 Testbench Code

```
`timescale 1ps/1ps
`include "reg_file.sv"

module reg_file_tb;
    logic [3:0] RA1, RA2, WA;
    logic clk, write_enable;
    logic [7:0] ALUResult, RD1, RD2, cpu_out;
    reg_file dut (RA1, RA2, WA, ALUResult, clk, write_enable, RD1, RD2, cpu_out);

    initial begin // Generate clock signal with 20 ns period
        clk = 0;
        forever #10 clk = ~clk;
    end

    initial begin // Apply stimulus
        $dumpfile("reg_file_tb.vcd");
    end
```

```

$dumpvars(0, reg_file_tb);
RA1 = 1; RA2 = 2; WA = 0; ALUResult = 5; write_enable = 0;
#15 write_enable = 1;
#20 WA = 1; ALUResult = 7;
#20 WA = 5; ALUResult = 13;
#20 write_enable = 0;
#10 RA2 = 5;
#10;
#10 WA = 15; write_enable = 1;
#10 ALUResult = 15;
#30;
$finish; // This system tasks ends the simulation
end

initial begin // Response monitor
    $monitor ("t = %3d, t_RA1 = %d t_RA2 = %d t_WA = %d ALUResult = %d t_clk = %d
        t_write_enable = %d t_RD1 = %d t_RD2 = %d t_cpu_out = %d",
        $time, RA1, RA2, WA, ALUResult, clk, write_enable, RD1, RD2, cpu_out);
end
endmodule

```

2.3 Simulations

The simulation results using Icarus Verilog is as below:

```

t = 0, RA1 = 1 RA2 = 2 WA = 0 ALUResult = 5 clk = 0 write_enable = 0 RD1 = x RD2 = x cpu_out = x
t = 10, RA1 = 1 RA2 = 2 WA = 0 ALUResult = 5 clk = 1 write_enable = 0 RD1 = x RD2 = x cpu_out = x
t = 15, RA1 = 1 RA2 = 2 WA = 0 ALUResult = 5 clk = 1 write_enable = 1 RD1 = x RD2 = x cpu_out = x
t = 20, RA1 = 1 RA2 = 2 WA = 0 ALUResult = 5 clk = 0 write_enable = 1 RD1 = x RD2 = x cpu_out = x
t = 30, RA1 = 1 RA2 = 2 WA = 0 ALUResult = 5 clk = 1 write_enable = 1 RD1 = x RD2 = x cpu_out = x
t = 35, RA1 = 1 RA2 = 2 WA = 1 ALUResult = 7 clk = 1 write_enable = 1 RD1 = x RD2 = x cpu_out = x
t = 40, RA1 = 1 RA2 = 2 WA = 1 ALUResult = 7 clk = 0 write_enable = 1 RD1 = x RD2 = x cpu_out = x
t = 50, RA1 = 1 RA2 = 2 WA = 1 ALUResult = 7 clk = 1 write_enable = 1 RD1 = 7 RD2 = x cpu_out = x
t = 55, RA1 = 1 RA2 = 2 WA = 5 ALUResult = 13 clk = 1 write_enable = 1 RD1 = 7 RD2 = x cpu_out = x
t = 60, RA1 = 1 RA2 = 2 WA = 5 ALUResult = 13 clk = 0 write_enable = 1 RD1 = 7 RD2 = x cpu_out = x
t = 70, RA1 = 1 RA2 = 2 WA = 5 ALUResult = 13 clk = 1 write_enable = 1 RD1 = 7 RD2 = x cpu_out = x
t = 75, RA1 = 1 RA2 = 2 WA = 5 ALUResult = 13 clk = 1 write_enable = 0 RD1 = 7 RD2 = x cpu_out = x
t = 80, RA1 = 1 RA2 = 2 WA = 5 ALUResult = 13 clk = 0 write_enable = 0 RD1 = 7 RD2 = x cpu_out = x
t = 85, RA1 = 1 RA2 = 5 WA = 5 ALUResult = 13 clk = 0 write_enable = 0 RD1 = 7 RD2 = 13 cpu_out = x
t = 90, RA1 = 1 RA2 = 5 WA = 5 ALUResult = 13 clk = 1 write_enable = 0 RD1 = 7 RD2 = 13 cpu_out = x
t = 100, RA1 = 1 RA2 = 5 WA = 5 ALUResult = 13 clk = 0 write_enable = 0 RD1 = 7 RD2 = 13 cpu_out = x
t = 105, RA1 = 1 RA2 = 5 WA = 15 ALUResult = 13 clk = 0 write_enable = 1 RD1 = 7 RD2 = 13 cpu_out = x
t = 110, RA1 = 1 RA2 = 5 WA = 15 ALUResult = 13 clk = 1 write_enable = 1 RD1 = 7 RD2 = 13 cpu_out = 13
t = 115, RA1 = 1 RA2 = 5 WA = 15 ALUResult = 15 clk = 1 write_enable = 1 RD1 = 7 RD2 = 13 cpu_out = 13
t = 120, RA1 = 1 RA2 = 5 WA = 15 ALUResult = 15 clk = 0 write_enable = 1 RD1 = 7 RD2 = 13 cpu_out = 13
t = 130, RA1 = 1 RA2 = 5 WA = 15 ALUResult = 15 clk = 1 write_enable = 1 RD1 = 7 RD2 = 13 cpu_out = 15
t = 140, RA1 = 1 RA2 = 5 WA = 15 ALUResult = 15 clk = 0 write_enable = 1 RD1 = 7 RD2 = 13 cpu_out = 15

```

The simulation results using GTKWave is as following:

