

Introduction to Logic Design with SystemVerilog (continued)

In session 1, we studied the digital system design process, and then covered

- Structural modelling of digital circuits using SystemVerilog built-in primitives and user defined primitives (UDPs).
- We described hierarchical design using SystemVerilog
- Behavioural modelling of combinational logic
- Test benches

In this session, we will look at behavioural modelling of sequential logic with SystemVerilog.

6. Behavioural modelling of sequential logic

Besides modelling sequential logic systems with user defined primitives, as discussed previously, there are a number of ways their behaviour can be described in SystemVerilog:

- continuous assignment statements, and
- cyclic beviour.

6.1 Latches and Level-Sensitive Circuits in SystemVerilog

The level-sensitive storage mechanism of a latch can be modelled using continuous-assignment statements.

When feedback is used in a continuous-assignment statement with a conditional operator, a synthesis tool will infer the functionality of a latch and its hardware implementation.

Example

Write a SystemVerilog model of a latch using a continuous assignment statement with feedback

```
module Latch_CA (input logic data_in, enable,  
                 output logic q_out);  
  
    assign q_out = (enable) ? data_in : q_out;  
  
endmodule
```

6.2 Cyclic Behavioural Models of Flip-Flops and Latches; Edge Detection

Continuous-assignment statements are limited to modelling level-sensitive behaviour

i.e. combinational logic and transparent latches

They cannot model an element that has signal pulse edge-sensitive behaviour, such as a flip-flop.

Verilog uses a **cyclic behaviour** to model edge-sensitive functionality.

6.2 Cyclic Behavioural Models of Flip-Flops and Latches; Edge Detection

Cyclic behaviours are abstract – they do not use hardware to specify signal values. Instead, they execute procedural statements, just like the statements of an ordinary procedural program (e.g. Java).


They are called *cyclic*, because they keep re-executing, every time another edge occurs.

Cyclic behaviours can be used to model (and synthesise) both level-sensitive and edge-sensitive (synchronous) behaviour.

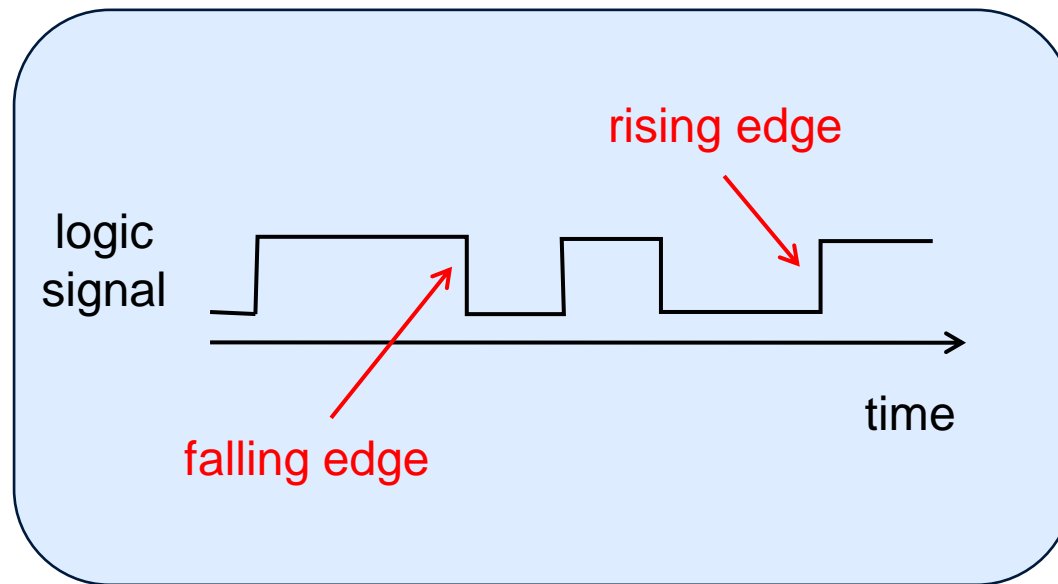6.2 Cyclic Behavioural Models of Flip-Flops and Latches; Edge Detection

Keywords: **posedge**, **negedge**

Edge semantics for rising (**posedge**) and falling (**negedge**) edges are built into Verilog.



6.2 Cyclic Behavioural Models of Flip-Flops and Latches; Edge Detection

The keyword **always_ff** in the Verilog model *df_behav* declares a cyclic behaviour corresponding to an edge-triggered flip-flop.

At every rising edge of *clk*, the behaviour's procedural statements execute, computing the value of *q* and storing it in memory.

The nonblocking, or concurrent, assignment operator **<=** will be explained later

```
module df_behav (input logic data, set, clk, reset,  
                 output logic q, q_bar);  
    assign q_bar = ~q;  
  
    always_ff @ (posedge clk)  
    begin  
        if (reset == 0) q <= 0;  
        else if (set == 0) q <= 1;  
        else q <= data;  
    end  
endmodule
```

6.2 Cyclic Behavioural Models of Flip-Flops and Latches; Edge Detection

The keyword **always_latch** can be used to declare a cyclic behaviour of level-sensitive, non-synchronous sequential logic. Unlike **always_ff**, **always_latch** does not use an event control expression, but is triggered by a change in a dependent variable.

For example, a model of a transparent latch is shown below.

```
module tr_latch (output logic q_out,  
                input logic enable, data);  
  
  always_latch  
  if (enable) q_out = data;  
  
endmodule
```


6.2 Cyclic Behavioural Models of Flip-Flops and Latches; Edge Detection

The keyword **always_comb** can be used to declare a combinational logic operation as a cyclic behaviour, as shown in the following example:

```
always_comb mywire = a & b
```

As with **always_latch**, **always_comb** is triggered by a change in a dependent variable, and does not use an event control expression.

6.2 Cyclic Behavioural Models of Flip-Flops and Latches; Edge Detection

The keywords **always_ff** can also be used to declare cyclic behaviours with an event-control expression based on more than one signal.

For example, in the functionality of an asynchronous flip-flop modelled in *asynch_df_behav*, the state of the flip-flop is sensitive to the rising edge of the clock, *clk*, but also to the falling edges of *reset* and *set*.

```

module asynch_df_behav (input logic    data, set, clk, reset,
                        output logic  q, q_bar);

assign q_bar = ~q;


always_ff @ (negedge set or negedge reset or posedge clk)
begin
    if (reset == 0) q<= 0;
    else if (set == 0) q<= 1;
    else q <= data;
end
endmodule

```

6.3 Non-blocking (Concurrent) Assignments in Cyclic Behaviours

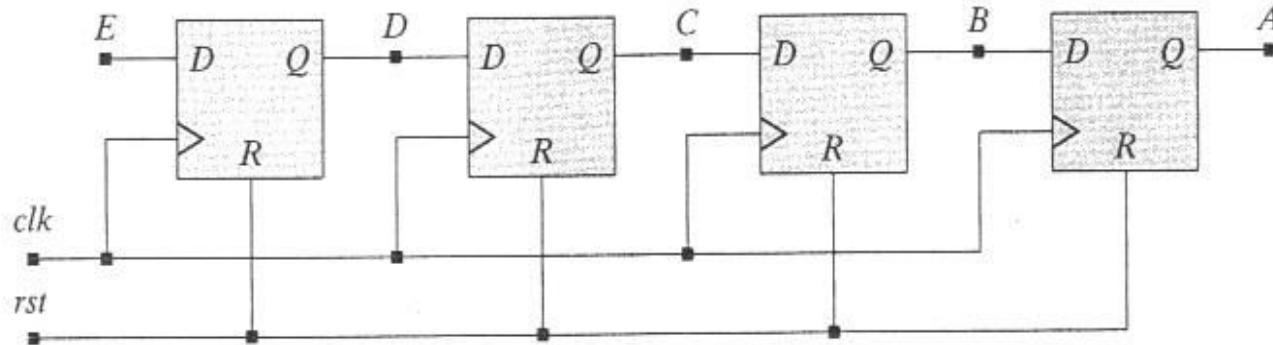Example

Write a SystemVerilog model of the 4-bit shift register shown below



```
module shiftreg_PA (input logic E, clk, rst,
                    output logic A);
```

```
logic    B, C, D;
```

```
    always_ff @ (posedge clk or posedge rst)
begin
```

```
    if (rst) begin A = 0; B = 0; C = 0; D = 0; end
```

```
    else begin
```

```
        A = B;
```

```
        B = C;
```

```
        C = D;
```

```
        D = E;
```

```
    end
```

```
end
```


```
endmodule
```

6.3 Non-blocking (Concurrent) Assignments in Cyclic Behaviours

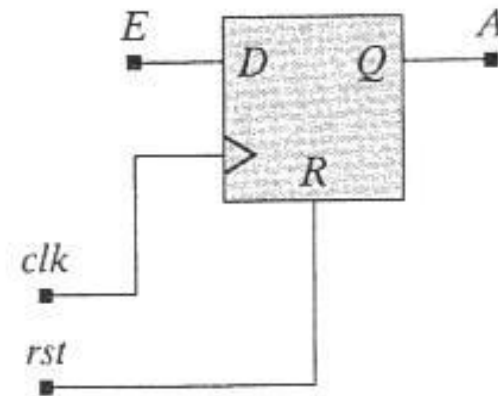Example (continued)

Now consider what happens if the order of the procedural assignments is reversed:

```
module shiftreg_PA (input logic E, clk, rst,  
                    output logic A);  
  
logic    B, C, D;  
  
always_ff @ (posedge clk or posedge rst) begin  
if (rst) begin A = 0; B = 0; C = 0; D = 0; end  
else begin  
    D = E;  
    C = D;  
    B = C;  
    A = B;  
end  
end  
endmodule
```



Synthesis tools would produce a single D-flip flop!

6.3 Non-blocking (Concurrent) Assignments in Dataflow/RTL Models

The assignment operator in the previous Example is the ordinary procedural assignment operator (=).

→ the statements are executed in the listed order, with storage of values occurring immediately after any statement executes., and before the next statement executes.

This means that the order in which the statements are listed can affect the functionality !

6.3 Non-blocking (Concurrent) Assignments in Cyclic Behaviours

An alternative SystemVerilog dataflow model uses **concurrent procedural assignments** (`<=`)

Also referred to as **non-blocking assignments**.

Non-blocking assignments effectively execute concurrently (in parallel), rather than sequentially

So the order in which they are listed has no effect.

Example

Repeat the previous Exercise - write a SystemVerilog model of the 4-bit shift register, but in this case using non-blocking assignments

```
module shiftreg_PA (input logic E, clk, rst,
                   output logic A);
logic B, C, D;

always_ff @ (posedge clk or posedge rst) begin
if (rst) begin A = 0; B = 0; C = 0; D = 0; end
else begin
    A <= B;    //    D <= E;
    B <= C;    //    C <= D;
    C <= D;    //    B <= C;
    D <= E;    //    A <= B;
end
end
endmodule
```

Here, the order in which the assignments are listed does not affect the functionality. The list of assignments in this module could be replaced with the commented (//) list, without any effect on the synthesised system.

6.3 Non-blocking (Concurrent) Assignments in Cyclic Behaviours

The general rule-of-thumb to follow is:

- in continuous assignments, use procedural assignments (=)
- in cyclic behaviours, use non-blocking assignments (<=)

6.4 Dataflow/RTL Models

Dataflow models describe concurrent operations on signals, usually in a synchronous machine, where


- computations on the signals stored in registers are initiated at the active edges of the clock, and then
- are completed in time to be stored in a register at the next active edge.

Dataflow models for synchronous machines are also called register transfer level (RTL) models.

6.5 Use of Conditional Statements (case, if)

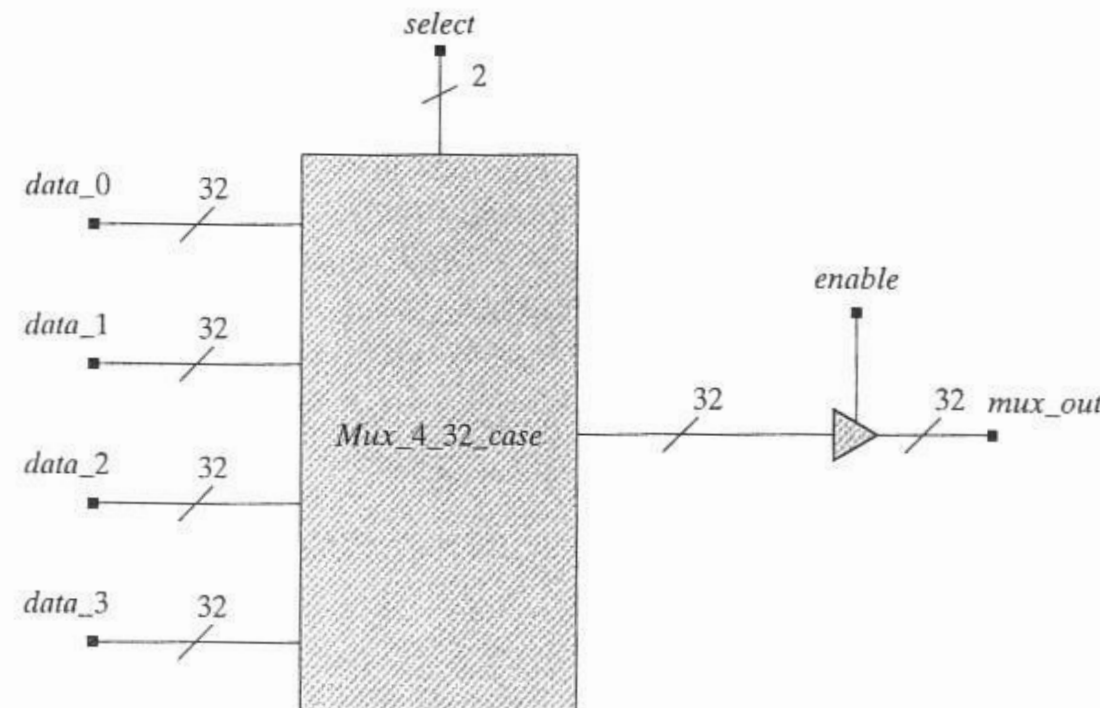Example Behavioural Model of a Multiplexer with case statements

Mux_4_32_case, on the following slide, is a behavioural model of the four-channel, 32-bit, multiplexer shown below, using the SystemVerilog **case** statement, which is similar to its counterpart in other languages (e.g. the **switch** statement in C).



Example (continued) Behavioural Model of a Multiplexer with case statements

```

module Mux_4_32_case (
input logic   [31:0] data_3, data_2, data_1, data_0,
input logic   [1:0]  select,
input logic  enable,
output logic [31:0] mux_out);

```

```

logic   [31:0] mux_int;

```

```

assign mux_out = enable ? mux_int : 32'bz;

```

```

always_comb

```

```

begin

```

```

    case (select)

```

```

        0:      mux_int = data_0;

```

```

        1:      mux_int = data_1;

```

```

        2:      mux_int = data_2;

```

```

        3:      mux_int = data_3;

```

```

        default: mux_int = 32'bx;

```

```

    endcase

```

```

end


```

```

endmodule

```

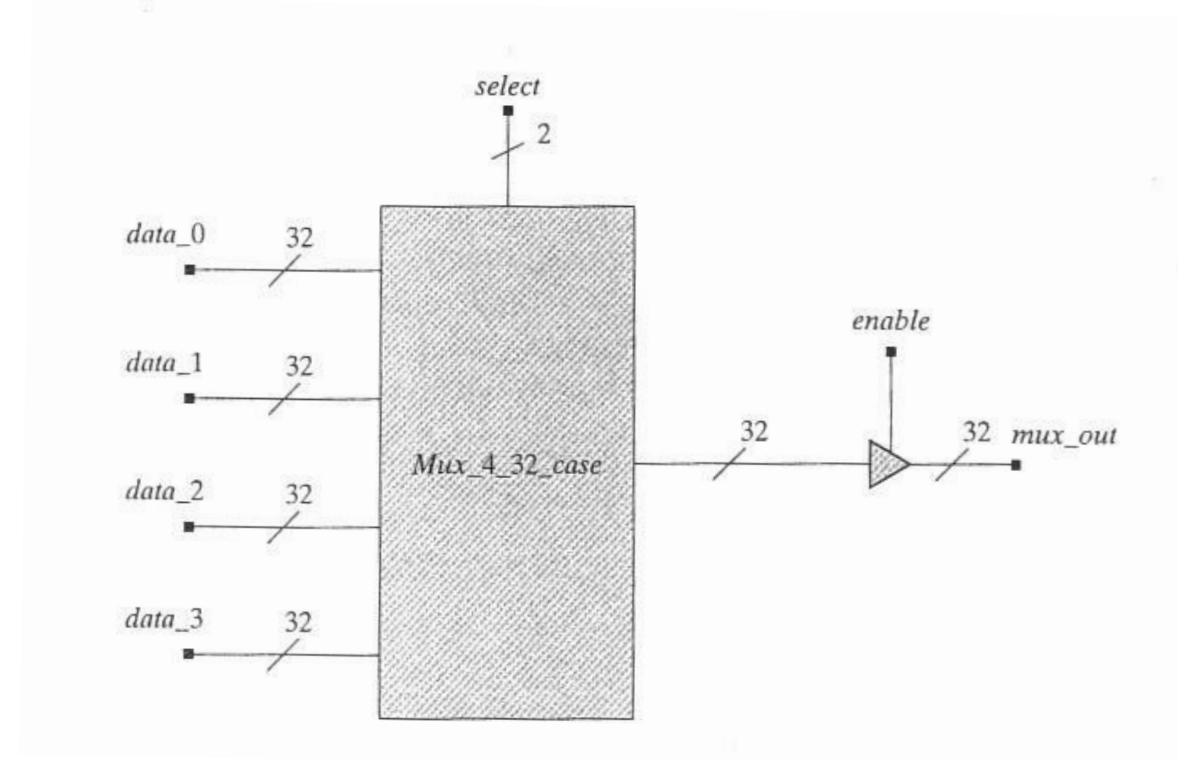//Note the use of the default case item, which covers cases
 // that might occur in simulation where a case statement
 // is not fully decoded for all possibilities.



Example Behavioural Model of a Multiplexer with nested conditional statements

Write a model of the multiplexer circuit considered in the previous example, but using nested conditional statements rather than case statements.

```


module Mux_4_32_if(
input logic  [31:0] data_3, data_2, data_1, data_0,
input logic  [1:0]  select,
input logic  enable,
output logic [31:0] mux_out);

logic  [31:0] mux_int;

assign mux_out = enable ? mux_int : 32'bz;

always_comb
begin
if (select == 0) mux_int = data_0; else
    if (select == 1) mux_int = data_1; else
        if (select == 2) mux_int = data_2; else
            if (select == 3) mux_int = data_3; else mux_int = 32'bx;
end
endmodule

```

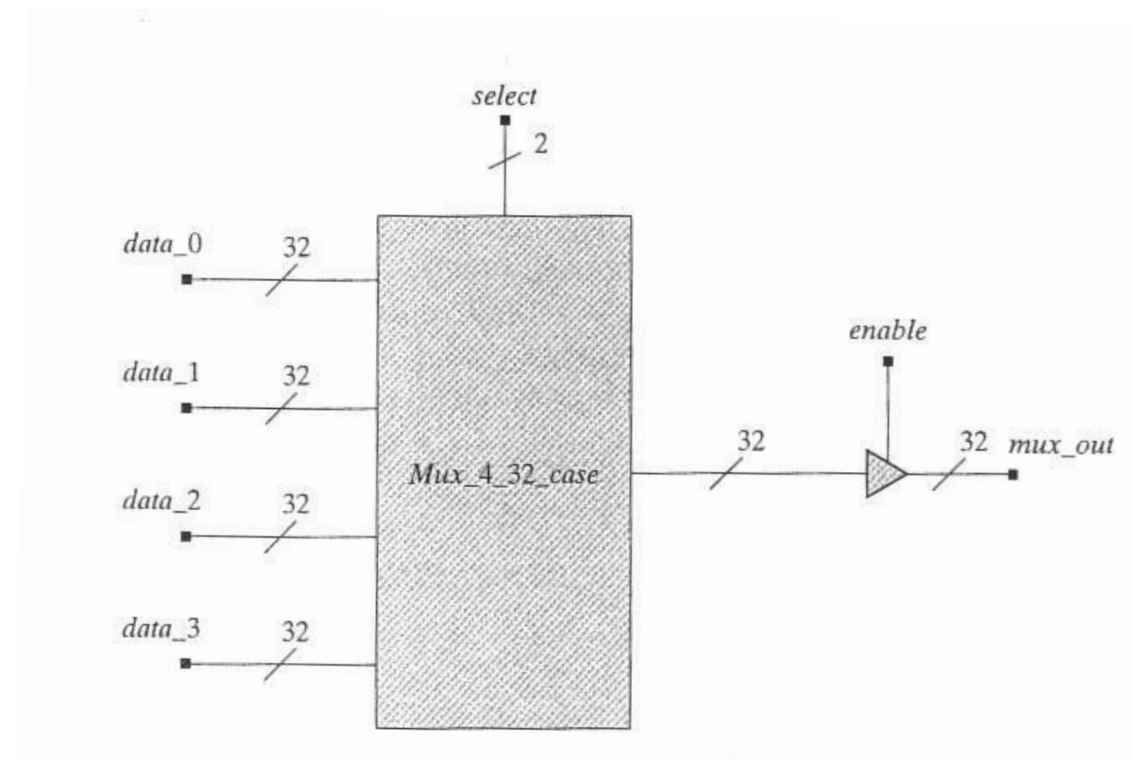

6.6 Modelling Digital Machines with Repetitive Algorithms

An algorithm for modelling the behaviour of a digital machine may execute some or all of its steps repeatedly in a given machine cycle, depending on whether the steps execute unconditionally or not.

SystemVerilog has four loop constructs for describing repetitive algorithms:

for, repeat, while, forever

Example A majority circuit using a **for** loop

A majority circuit outputs '1' if a majority of the bits of an input word are '1'. The model *Majority*, uses a **for** loop to count the input bits which are '1'.

```

module Majority(
input logic [2:0] Data,
output logic Y);

parameter    majority = 2;
reg    [2:0] count;
integer    k;

    always_comb
    begin
        count = 0;
        for (k = 0; k < 3; k = k + 1) begin
            if (Data[k] == 1) count = count + 1;
        end
        Y = (count >= majority);
    end
endmodule

```

This code models a combinational logic circuit with the truth table:

Data[2]	Data[1]	Data[0]	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

*Example Use of a **repeat** loop*

A repeat loop is used in the fragment of code below to initialise a memory array:

```
...  
word_address = 0;  
repeat (memory_size)  
  begin  
    memory[word_address] = 0;  
    word_address = word_address + 1;  
  end  
...
```

Example

The function *aligned_word* in *word_aligner* shifts (<< is the left-shift operator) an 8-bit word to the left until the most significant bit is a 1.

```
module word_aligner (input logic  [7:0]  word_in,
                    output logic [7:0]  word_out);


assign word_out = aligned_word(word_in);

function [7:0] aligned_word;
  input    [7:0]  word;
  begin
    aligned_word = word;
    if (aligned_word != 0)
      while (aligned_word[7] == 0) aligned_word = aligned_word << 1;
    end
  endfunction

endmodule
```

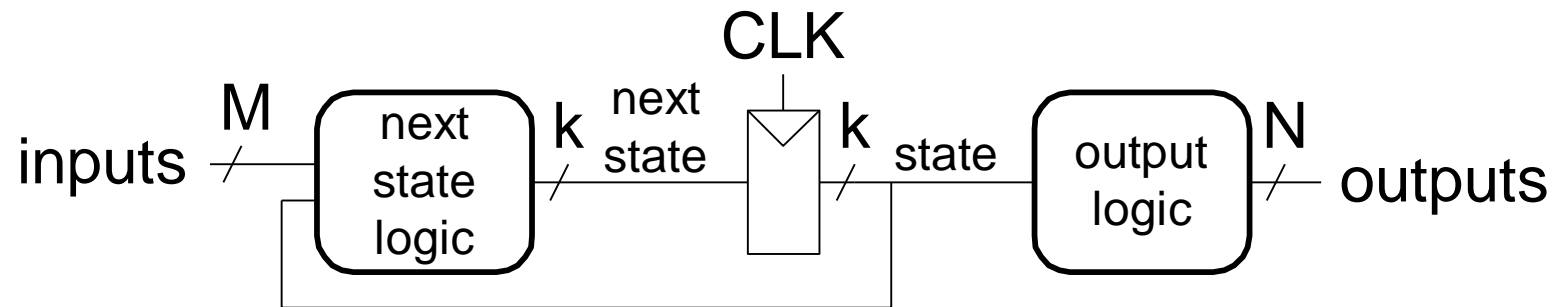
6.7 Finite State Machines (FSMs)


- **Three blocks:**
 - next state logic
 - state register
 - output logic



The state of the system must be held in an internal register. In SystemVerilog, the state can be represented by an enumerated type. The possible values of this type are the state names, and the name of the variable is given after the list of values. For example:

```
enum {s0, s1, s2, s3} state;
```

FSM Example1

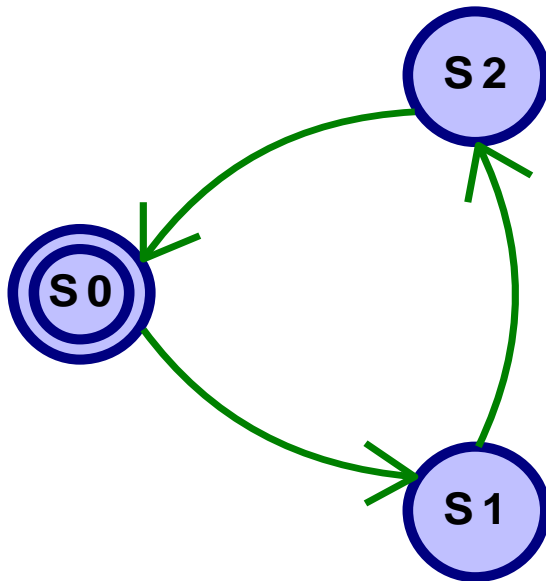

Output $q=1$ when state is S0, else $q=0$

The double circle indicates the reset state

```

module FSM_example1 (input logic clk,
reset,
                        output logic q);
  
```

```

  enum {s0, s1, s2} present_state,
next_state;
  
```

```

  // state register
  
```

```

always_ff @ (posedge clk, posedge reset)
  if (reset) present_state <= S0;
  else    present_state <= next_state;
  
```

```

  // next state logic
  
```

```

always_comb
  case (present_state)
    S0:    next_state = S1;
    S1:    next_state = S2;
    S2:    next_state = S0;
    default: next_state = S0;
  endcase
  
```


```

  // output logic
  
```

```

  assign q = (present_state == S0);
endmodule
  
```

FSM Example 2

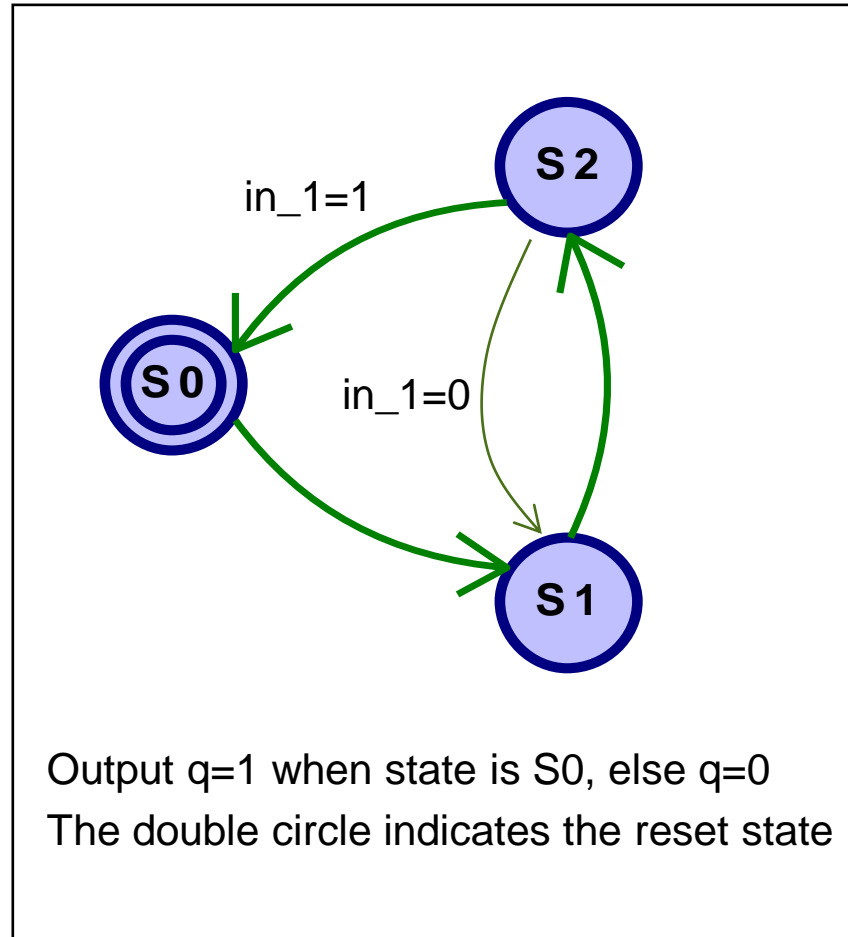

```

module FSM_example2 (input logic clk, reset,
in_1,

```

```

output logic q);

```

```

enum {s0, s1, s2} present_state, next_state;

```

```

// state register

```

```

always_ff @ (posedge clk, posedge reset)

```

```

    if (reset) present_state <= S0;

```

```

    else    present_state <= next_state;

```

```

// next state logic

```

```

always_comb

```

```

    case (present_state)

```

```

        S0:    next_state = S1;

```

```

        S1:    next_state = S2;

```

```

        S2:    if (in_1)
                next_state = S0;

```

```

        else

```

```

            next_state = S1;

```

```

        default: next_state = S0;

```

```

    endcase

```

```

// output logic

```

```

    assign q = (present_state == S0);

```

```

endmodule

```

Common mistakes to avoid in SystemVerilog coding

module <name> (<port list>;

<Local variables declared>

Other modules instantiated

Netlist of primitives

Single pass behaviour – **initial**

Continuous assignment statement - **assign**

Cyclic behavior – e.g. **always_ff**, **always_latch**

endmodule

All the blocks are running simultaneously

The order of the blocks is not important

Do not mix up the styles of the blocks! Each block of code has to be one of these types.

For example:

Don't use continuous assignments (**assign**) inside cyclic behaviours (e.g. **always_ff**)

Don't instantiate modules or primitives inside continuous assignment statements, single pass behaviours or cyclic behaviours

Common mistakes to avoid in SystemVerilog coding

Examples of incorrect code:

```
always_ff @ (posedge clock)
begin
  assign y = a & b;
end
```




Can't use a continuous assignment statement inside a cyclic behaviour

```
always_latch
begin
  and (y, a, b);
  module my_circuit (w, c, d);
end
```



Can't instantiate primitives or other modules inside a cyclic behaviour

```
assign xor (t, e, f);
```

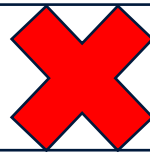

Can't instantiate primitives or other modules inside a continuous assignment statement