 


ELEC0010 Digital Design – SystemVerilog coding exercises




Write SystemVerilog models of the circuit shown above, using:

- (i) a netlist of built-in primitives.
- (ii) a user-defined primitive (UDP)
- (iii) a Boolean expression within a continuous assignment statement

Model solutions are on the next pages.

Solutions

 - (i) Netlist of built-in primitives. Start by defining internal variables, D, E, and F, as shown in the figure below.



```

module circuit_model1 (input logic a, b, c,
                       output logic y);

```

```

logic d, e, f; // Internal variables

```

```

or (y, e, f);
and (e, a, b);
and (f, d, c);
not (d, b);

```

```

endmodule

```

- (ii) User define primitive (UDP). This method uses the truth table description of the circuit.

```

primitive circuit_model2 (y, a, b, c);
output y;
input a, b, c;

```

```

table
// a b c : y
  0 0 0 : 0
  0 0 1 : 1
  0 1 0 : 0
  0 1 1 : 0
  1 0 0 : 0
  1 0 1 : 1
  1 1 0 : 1
  1 1 1 : 1
endtable
endprimitive

```

- (iii) A Boolean expression within a continuous assignment

```
module circuit_model3 (input logic a, b, c,  
                      output logic y);  
  
assign y = (a & b) | (~b & c);  
  
endmodule
```